

- 3 (a) By reference to energy transfers, distinguish between electromotive force (e.m.f.) and potential difference (p.d.).

.....

.....

.....

.....

..... [2]

- (b) A circuit is set up as shown in Fig. 3.1.

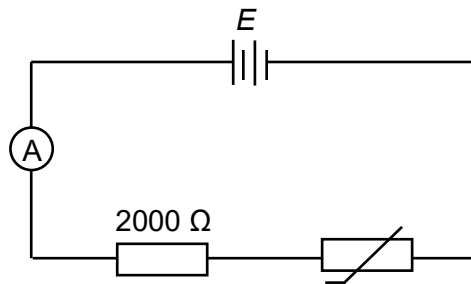


Fig. 3.1

The battery source of e.m.f. E is found to provide 2.4×10^5 J of electrical energy to the 2000Ω resistor and the NTC thermistor when a charge of 2.2×10^4 C passes through the ammeter. At room temperature, the NTC thermistor has a resistance of 1800Ω .

For the thermistor at room temperature,

- (i) show that E is 11 V.

[1]

- (ii) determine the time taken for a charge of 2.2×10^4 C to pass through the ammeter.

time = s [2]

(iii) determine the fraction of power dissipated in the thermistor.

fraction = [2]

- (c) A uniform resistance wire PQ of length 1.2 m is subsequently connected across the resistor and the thermistor, as shown in Fig. 3.3. A sensitive voltmeter is connected between point Y and a moveable contact M on the wire.

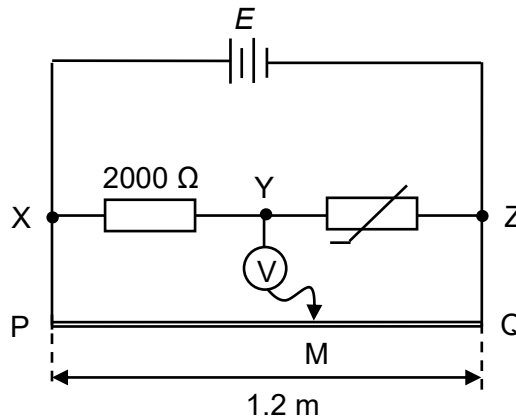


Fig. 3.3

- (i) At room temperature, the contact M is moved along PQ until the voltmeter shows zero reading.

Calculate the length of wire between M and Q.

length = m [2]

- (ii) State and explain the effect, if any, on the length of the wire between M and Q for the voltmeter to remain at zero deflection if each of the following changes takes place independently.

1. The thermistor is warmed slightly.

.....

.....

.....

.....

..... [2]

2. A uniform wire of the same resistivity but with a bigger cross sectional area is used to replace PQ.

.....

.....

.....

.....

..... [2]

[Total: 13]