

- 4 (a) In a laboratory, a circuit is set up as shown in Fig. 4.1. Cell A has an electromotive force (e.m.f.) of 2.0 V and negligible internal resistance. XY is a uniform wire of length 100.0 cm and resistance 5.0  $\Omega$ .

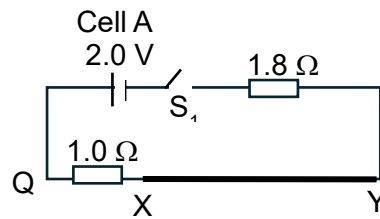


Fig. 4.1

- (i) Explain what is meant by *electromotive force* (e.m.f.) of 2.0 V.

.....


.....

.....[1]

- (ii) Calculate the current in the 1.0  $\Omega$  resistor and wire XY when switch  $S_1$  is closed.

current = ..... A [1]

- (b) A second circuit which contains Cell B of e.m.f. 1.2 V and negligible resistance is connected to the circuit in (a) at Q and P.

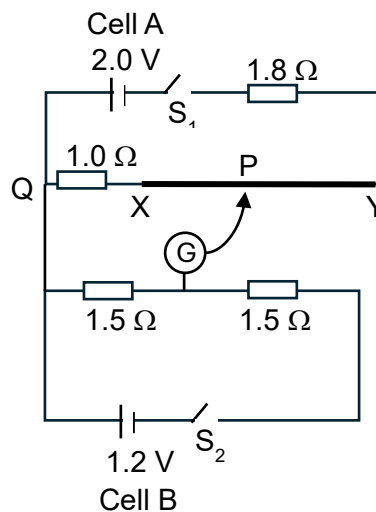

**Fig. 4.2**

- (i) Calculate the balance length  $XP$  required to produce a zero deflection on the galvanometer when both switches  $S_1$  and  $S_2$  are closed.

length = ..... m [3]

- (ii) Describe and explain how the balance length  $XP$  will be different if the  $1\ \Omega$  resistor is replaced with a  $1\ \text{k}\Omega$  resistor.

.....  
.....  
.....  
.....[2]

- (iii) If both  $1.5\ \Omega$  resistors are replaced with identical LDRs, describe and explain how the balance length  $XP$  will be different as the light intensity in the laboratory decreases.

.....  
.....  
.....  
.....[2]

[Total: 9]

