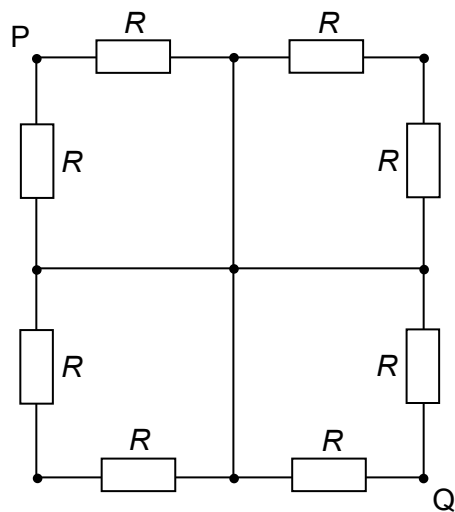


- 22** Eight identical resistors, each of resistance R , are connected in a network as shown below.



What is the effective resistance between terminals P and Q ?

- A** $0.5R$ **B** R **C** $2R$ **D** $4R$