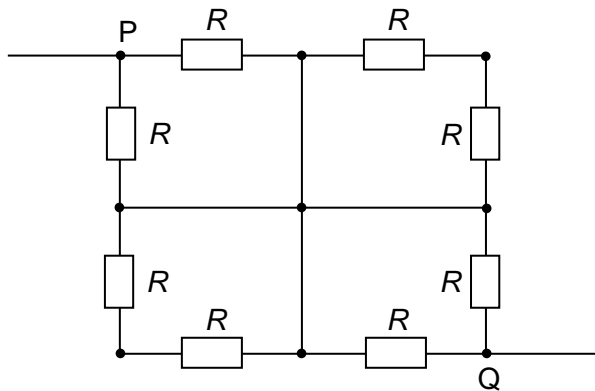


- 23 Eight identical resistors, each of resistance R , are connected in a network as shown below.



What is the effective resistance between the terminals P and Q?

A $\frac{R}{8}$

B $\frac{R}{2}$

C R

D $2R$