

- 4 A cell P, a fixed resistor  $R$  and a uniform resistance wire AB are connected in a circuit as shown in Fig. 4.1.

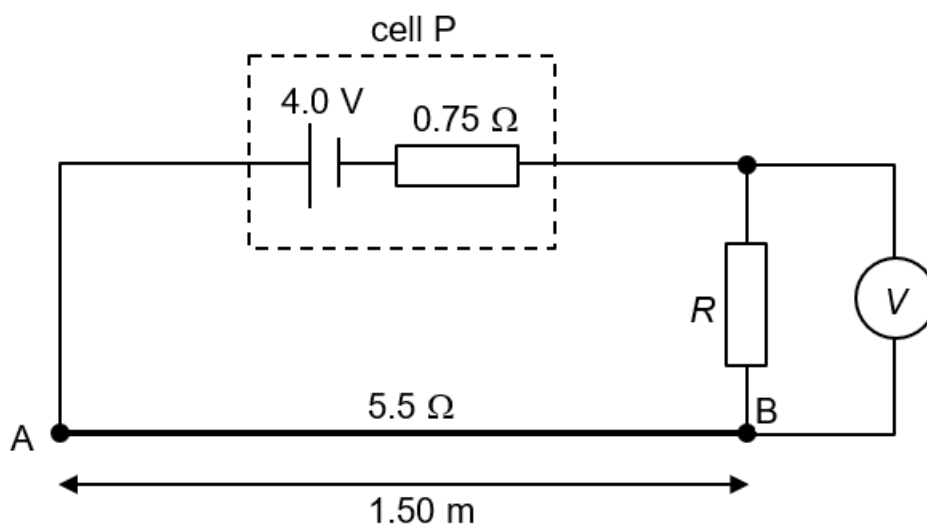


Fig. 4.1

Cell P has e.m.f. 4.0 V and internal resistance  $0.75\ \Omega$ . Wire AB has length 1.50 m and resistance  $5.5\ \Omega$ . The voltmeter reads 1.3 V.

- (a) Show that the potential difference across AB is 2.4 V.

[2]

- (b) A cell Q and a sensitive ammeter are connected to the circuit in Fig. 4.1, as shown in Fig. 4.2.

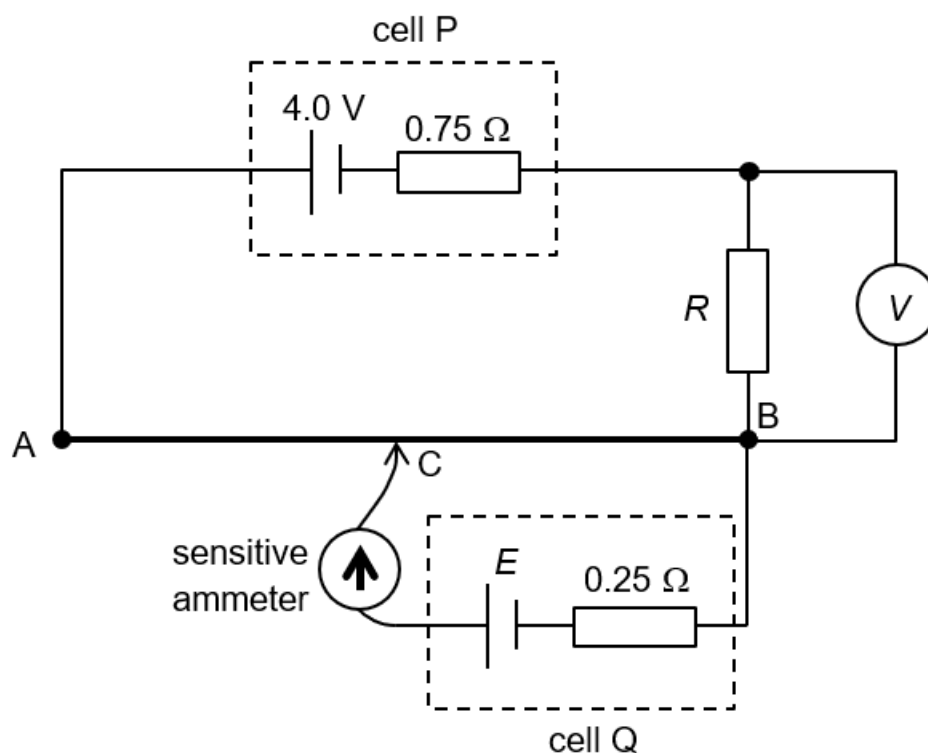


Fig. 4.2

Cell Q has e.m.f.  $E$  and internal resistance  $0.25\ \Omega$ . The ammeter reads zero when the length of AC is  $0.56\text{ m}$ .

- (i) Determine  $E$ .

$E = \dots\dots\dots\text{ V}$  [2]

- (ii) There is a reading on the ammeter when the connection C is shifted closer to A. State and explain the direction of the current across cell Q.

.....

.....

.....

..... [2]

- (c) The resistance wire AB is detached from the circuit and wound in a circular manner such that there are 2 semi-circular turns above and 3 semi-circular turns below XY as shown in Fig. 4.3.

X and Y are two metallic fasteners with negligible resistance. They are used to secure the wire so that the distance between X and Y is the diameter of the coil.

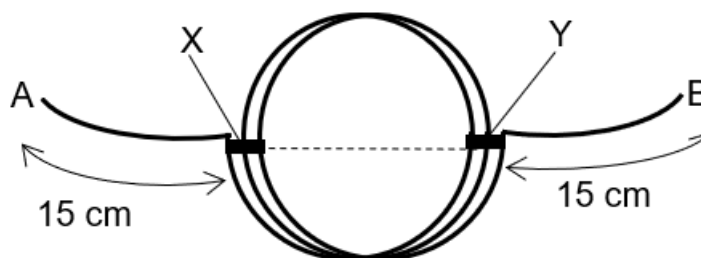


Fig. 4.3

- (i) Show that the resistance of wire AB when coiled in this manner is  $1.3 \Omega$ .

[2]

- (ii) An e.m.f. source is again connected across AB. State and explain whether the drift velocity of electrons is greater in section AX or section XY.

.....

.....

.....

.....

[2]