

- 7 A 240 V a.c. mains is connected to a step-down transformer, a full wave rectifier and a motor as shown in Fig. 7.1. The electric motor requires an operating peak power of 6.6 W.

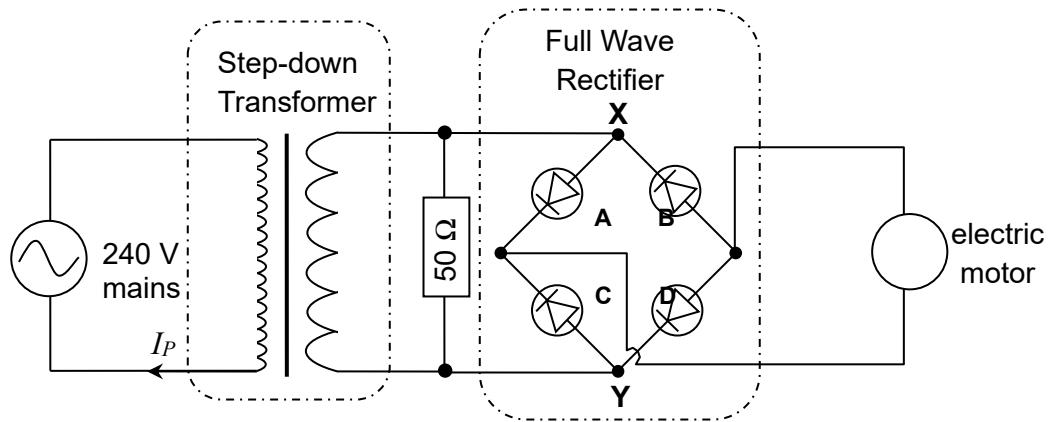


Fig. 7.1

The variation of potential difference across the $50\ \Omega$ resistor with time is shown in Fig. 7.2.

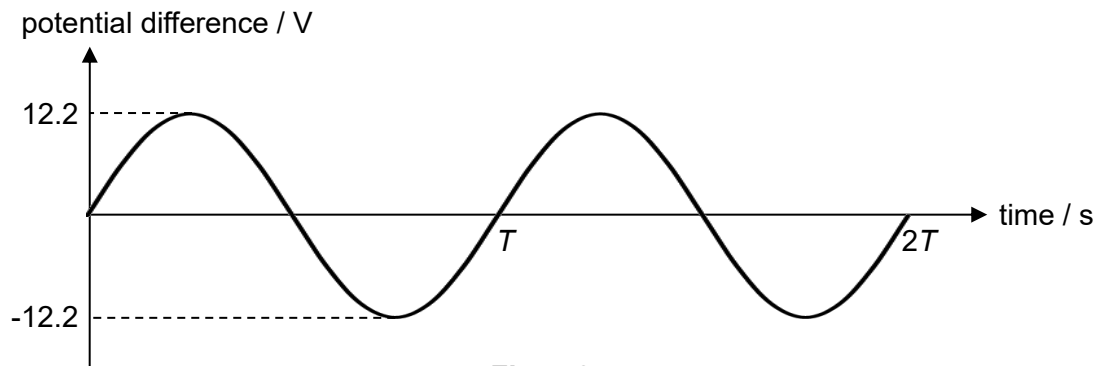


Fig. 7.2

- (a) Determine the turns ratio of primary coil to secondary coil in the step-down transformer.

turns ratio = [2]

- (b) (i) For half a period T , the potential at X is higher than that at Y.

On Fig. 7.1, draw an arrow to indicate the direction of current, if any, across the four diodes A, B, C and D during this half of a period.

[1]

- (ii) Sketch, on Fig. 7.3, the variation of potential difference across the electric motor with time. Numerical calculation is not required.

[1]

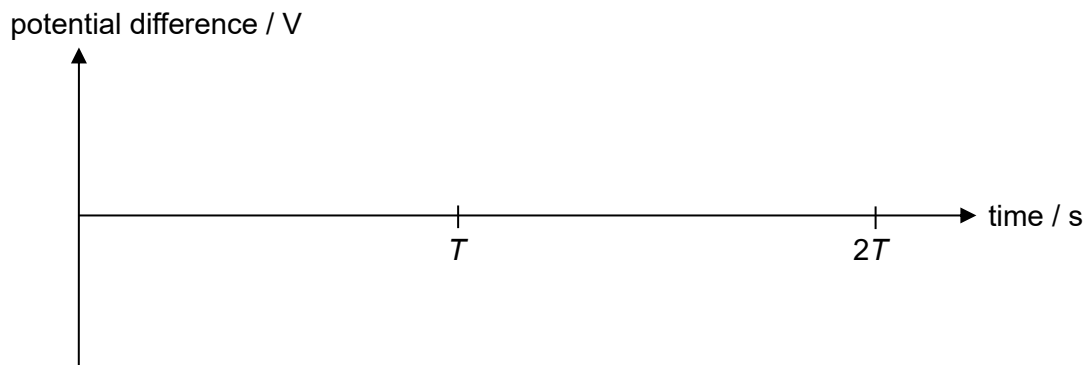


Fig. 7.3

- (iii) Hence, sketch, on Fig. 7.4, the variation of output power of the step-down transformer with time when the electric motor is operating at its normal operating power. Include appropriate values in the output power axis.



$$\frac{I}{T}$$

$$\frac{I}{2T}$$

Fig. 7.4

[2]

- (c) Given that the transformer is 80% efficient, determine the r.m.s. current flowing through the primary coil.

current = A [2]

[Total: 8]