
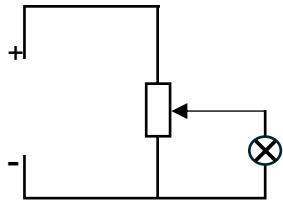


- 21** A lamp is connected to a power supply of negligible internal resistance. Which circuit could not be used as a practical means to vary the voltage across the lamp?


**A**

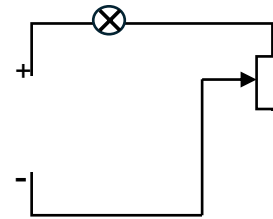

**B**



**C**

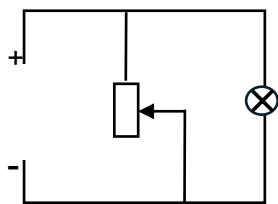

**D**

