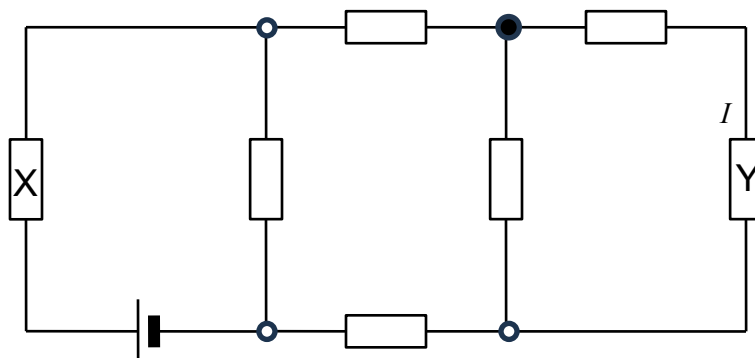


- 21 A battery of negligible internal resistance is connected to a network of identical resistors as shown.



If the current in resistor Y is I , what is the current in resistor X?

- A** $19 I$ **B** $11 I$ **C** $7 I$ **D** I

