

- 28** A lamp is rated at 60 W for a 240 V a.c. power supply. The lamp is connected to the power supply.

What is the peak current through the lamp?

A 0.25 A

B 0.35 A

C 4.0 A

D 5.7 A