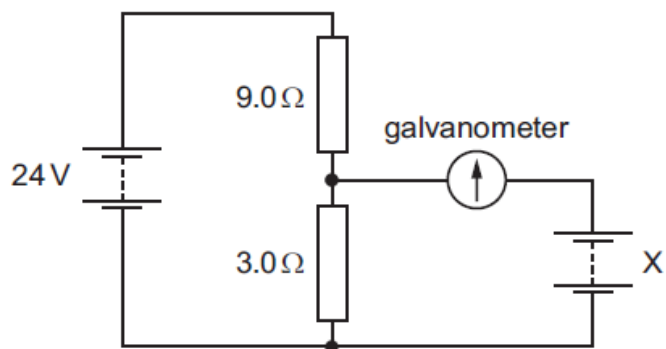


- 23** A circuit contains two batteries, each of negligible internal resistance, and two resistors as shown.



The galvanometer has a current reading of zero.

What is the electromotive force (e.m.f) of battery X?

- A** 6.0 V **B** 8.0 V **C** 16.0 V **D** 18.0 V