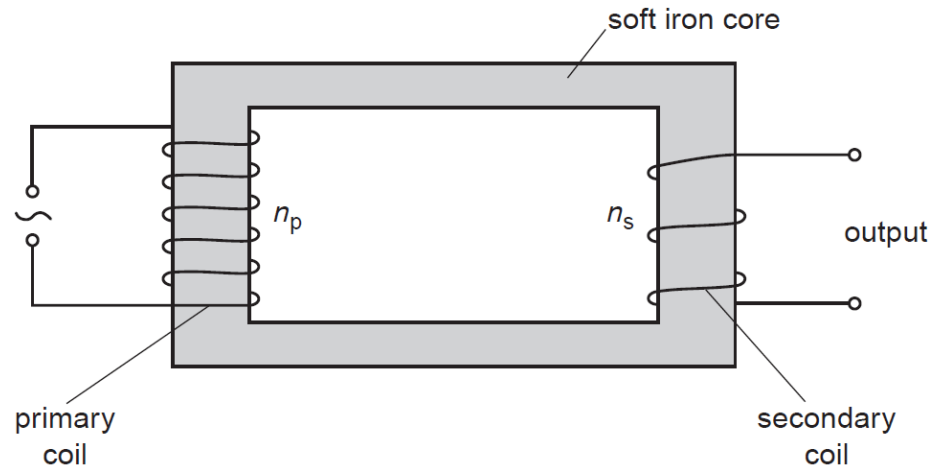


- 5 Fig. 5.1 shows a simple transformer.



**Fig. 5.1**

The transformer with 4200 turns in the primary coil is connected to a 230 V mains supply. The e.m.f. across the output is 12 V. Assume the transformer is 100% efficient.

- (a) Calculate the number of turns in the secondary coil.

number of turns = ..... [2]

- (b) The transformer output terminals are connected to a lamp using leads that have a total resistance of  $0.35\ \Omega$ . The p.d. across the lamp is 11.8 V. Calculate

- (i) the r.m.s. current in the leads connected to the lamp,

current = ..... A [2]

- (ii) the maximum power dissipated in the leads.

power = ..... W [2]

[Total: 6]

**BLANK PAGE**

