

- 25** A 240 V supply is connected to an ideal transformer. The output of the transformer is connected to five 12 V, 24 W lamps connected in parallel. The lamps are operating normally.

What is the current drawn from the supply?

- A** 0.10 A **B** 0.50 A **C** 2.0 A **D** 10.0 A