

3 Fig. 3.1 shows the current-voltage (I - V) characteristics of two resistors R and X.

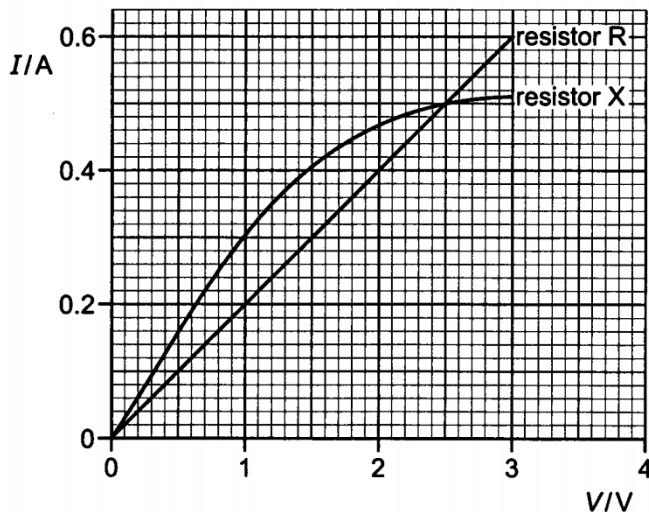


Fig. 3.1

The two resistors are connected in series with a cell of negligible internal resistance as shown in Fig. 3.2. The e.m.f. of the cell is 2.5 V.

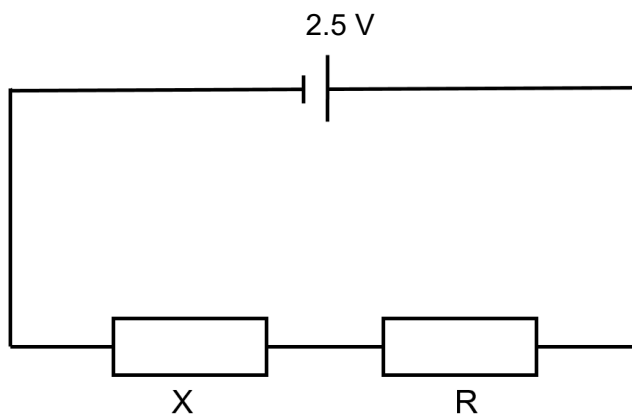


Fig. 3.2

(a What is meant by the term *e.m.f.* of a cell?

)

...

.....

.....

.

.....[2

]

(Describe and explain how the resistance of resistor X varies with increasing potential difference with reference to the motion of the electrons.

)

.....

.

.....

.

.....

.

.....

.

.....[3]

]

(c (i) Using Fig. 3.1, determine the current passing through resistor X.
) Show your working clearly.

current = A [3]

(ii) State

1. the resistance of X

resistance of X = Ω [1]

2. the resistance of R

resistance of R = Ω [1]

[Total: 10]

