

- 4 (a) Explain the term root mean square (r.m.s.) value of a current.
..... [1]

- (b) An a.c. generator consists of a rectangular coil of 800 turns with the dimensions $5.0\text{ cm} \times 8.0\text{ cm}$ in a uniform magnetic field of magnitude 0.50 T . The coil has a resistance of 0.60Ω and it is connected to an external load of resistance 11.4Ω in a complete circuit. The coil is rotating at a constant speed of 240 revolutions per minute.

- (i) Given that for a rotating coil, the e.m.f. induced is $NBA\omega \sin(\omega t)$, where N is the number of turns, B is the magnetic field strength, A is the cross-sectional area of the coil, ω is the angular velocity, and t is time, calculate the maximum voltage produced by this generator.

maximum voltage = V [2]

- (ii) Calculate the maximum current through the external load.

maximum current = A [1]

- (iii) Calculate the r.m.s. current through the external load.

r.m.s. current = A [1]

- (iv) On the axes below, sketch a graph of power dissipated, P in the external load against time, t for 2 cycles of the a.c. current. Include the value of the maximum power in the sketch. [3]



[Total: 8]

