

- 6 A battery of electromotive force (e.m.f.) 9.0 V and negligible internal resistance is connected to resistors P and Q, a light dependent resistor (LDR) and ammeters A_1 and A_2 , as shown in Fig. 6.1.

The resistance of P is $4.0\text{ k}\Omega$ and the resistance of Q is $6.0\text{ k}\Omega$.

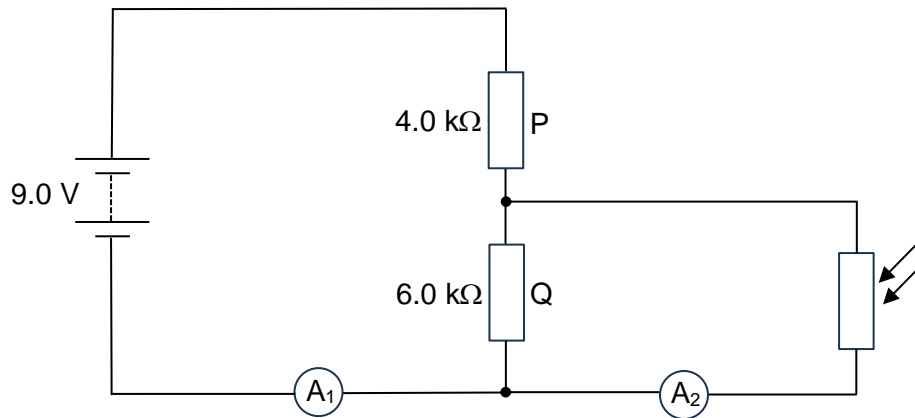


Fig. 6.1

- (a) The intensity of the light incident on the LDR is such that the resistance of the LDR is $8.0\text{ k}\Omega$.

Determine the current reading on

- (i) ammeter A_1 ,

current = A [2]

- (ii) ammeter A_2 .

current = A [2]

- (b) The intensity of the light incident on the LDR is lowered.

Explain the following changes:

- (i) The potential difference across Q increases.

.....

.....

.....

.....

..... [2]

- (ii) The current reading on ammeter A_2 decreases.

.....

.....

.....

.....

..... [2]