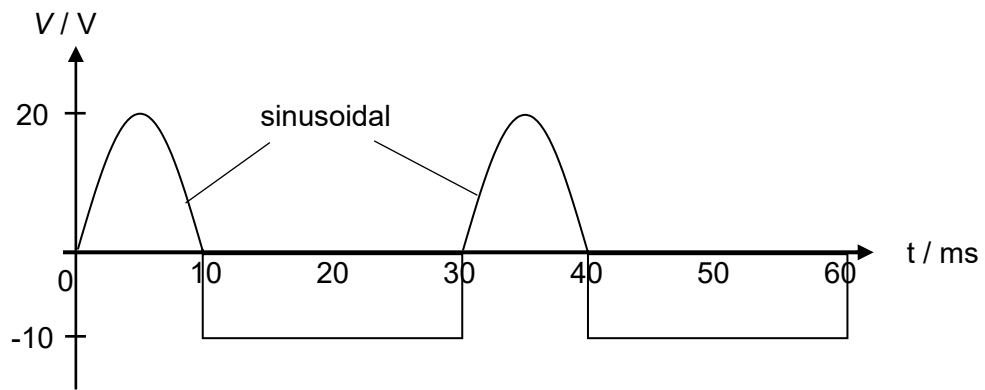


- 27** An alternating voltage is connected to a resistor of resistance $5.0\ \Omega$.



What is the mean power dissipated by the resistor?

- A** 16 W **B** 27 W **C** 120 W **D** 800 W