
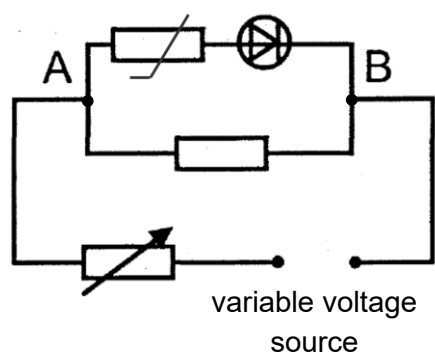


- 21 A circuit is set up as shown below.

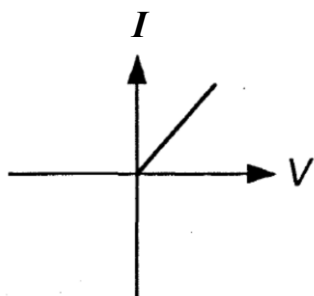


Which of the following  $I$ - $V$  graphs represent the current through, and voltage across, points AB?


A



B

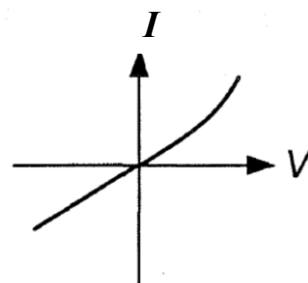

C

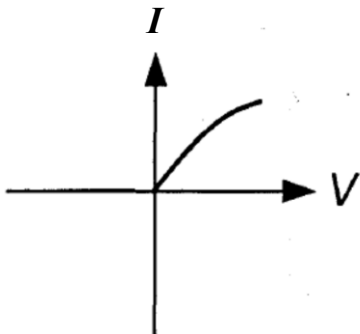

D

