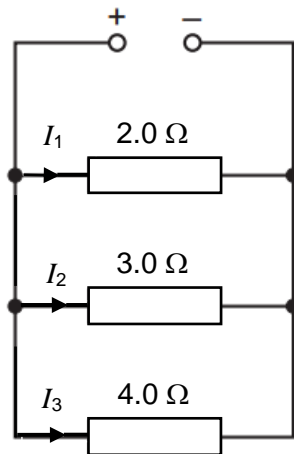


- 22** Three resistors are connected in parallel across a power supply, as shown.



What is the ratio of the currents $I_1 : I_2 : I_3$?

A 3 : 4 : 6

B 6 : 4 : 3

C 9 : 16 : 18

D 18 : 16 : 9