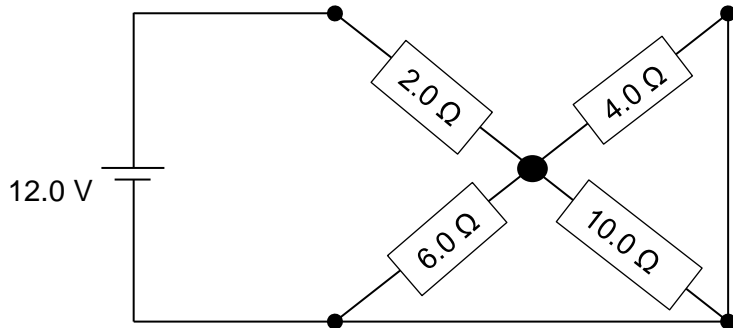


- 23 A cell of e.m.f. 12.0 V with negligible internal resistance is connected to 4 resistors.



What is the current flowing through the  $10.0\ \Omega$  resistor?

- A** 0.59 A                      **B** 1.0 A                      **C** 5.3 A                      **D** 11 A