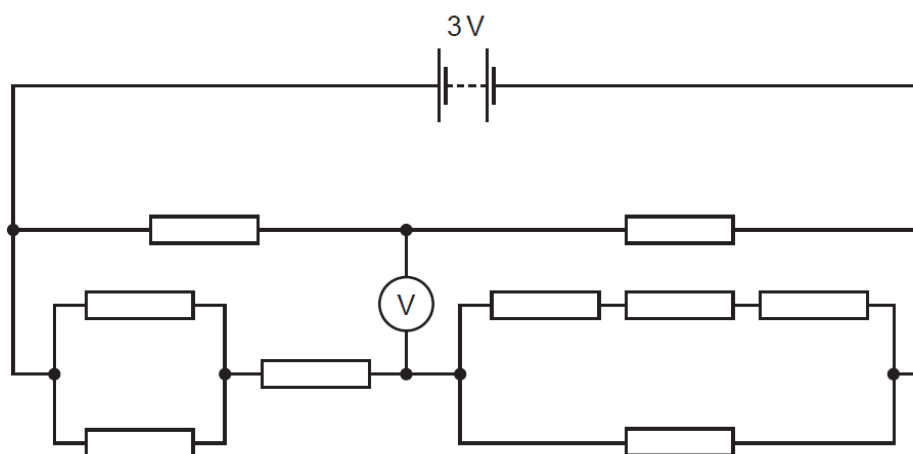


- 22** A circuit is set up as shown, supplied by a 3 V battery. All resistances are $1\text{ k}\Omega$.



What will be the reading on the voltmeter?

- A** 0 V **B** 0.5 V **C** 1.0 V **D** 1.5 V