

- 5 (a) Define *potential difference* between two points in a circuit.

.....  
 .....  
 .....  
 ..... [1]  
 .....

- (b) A thermistor and a variable resistor are connected in a potential divider circuit as shown in Fig. 5.1.

The battery has an e.m.f. of  $E$ , the thermistor has a resistance  $R_T$  and the variable resistor has a resistance  $R_V$ .

This circuit is used to activate an alarm system whenever the ambient temperature rises to a certain value. The alarm bell will sound if the potential difference across it increases beyond the pre-set value.

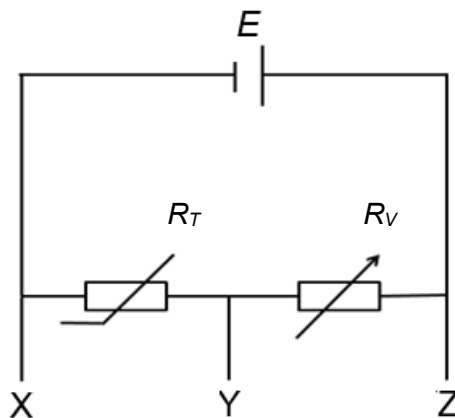


Fig. 5.1

- (i) State an expression for the potential difference across the variable resistor in terms of  $E$ ,  $R_T$  and  $R_V$ . [1]

- (ii) State and explain across which two terminals, XY or YZ, the alarm bell should be connected to the circuit in Fig. 5.1.

.....  
.....

.....  
.....

.....  
.....

.....  
.....

..... [2]

- (iii) State and explain the purpose of the variable resistor in the circuit.  
)

.....  
.....

.....  
.....

.....  
.....

..... [2]

- (c) Fig. 5.2 shows a potentiometer circuit consisting of a 100 cm length of wire AB and a driver cell  $E_1$  of e.m.f. 2.0 V and of negligible internal resistance.


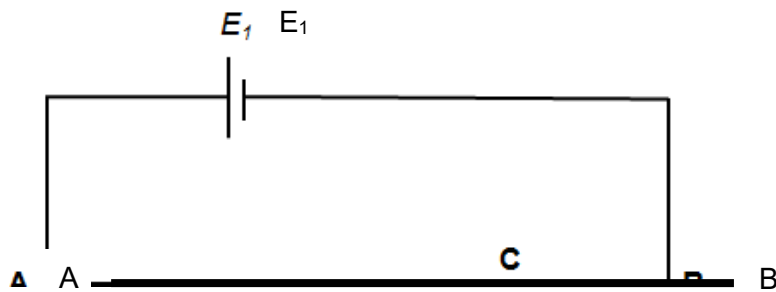


Fig. 5.2

- (i) State the value of the potential gradient along AB.

potential gradient = ..... V cm<sup>-1</sup> [1]

- (ii) A circuit consisting of a cell  $E_2$  and a variable resistor  $R$  is now connected to the potentiometer as shown in Fig. 5.3.

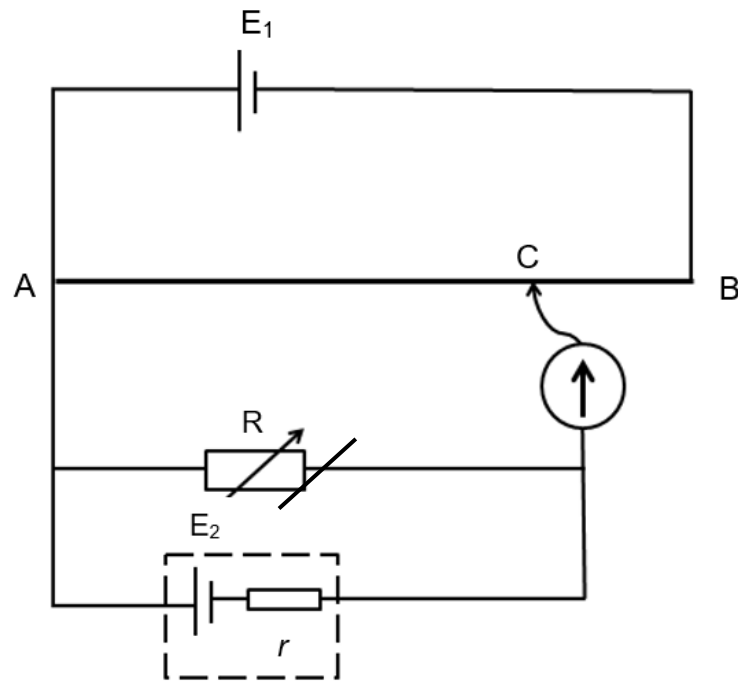

**Fig. 5.3**

The resistance of  $R$  is set to  $10.0\ \Omega$  and the sliding contact  $C$  is adjusted until there is no current flowing in the galvanometer. The length  $AC$  is found to be  $60.0\text{ cm}$ .

The resistance of  $R$  is now set to  $3.0\ \Omega$  and the experiment is repeated. The length  $AC$  is now  $54.0\text{ cm}$ .

Calculate the e.m.f. and internal resistance  $r$  of cell  $E_2$ .

e.m.f. of cell  $E_2$  = ..... V

internal resistance of cell  $E_2$  = .....  $\Omega$  [5]