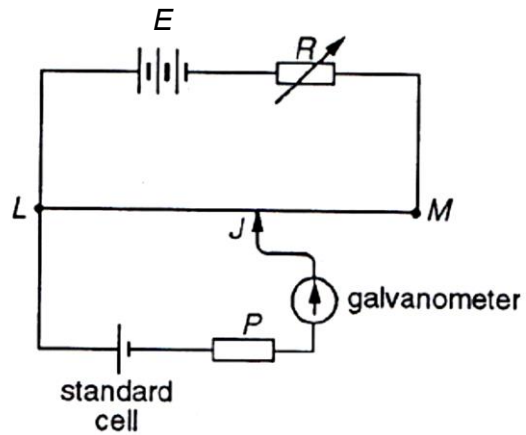


- 23 No balance point can be found for the potentiometer shown below.



Which of the following may allow a balance point to be found?

- A increasing the resistance of the rheostat R .
- B replacing the resistance wire LM with one of higher resistance.
- C reversing the polarity of the driver cell E .
- D replacing the resistor P with one of higher resistance.