

- 24** A battery of e.m.f. 10 V with an internal resistance of $2.0\ \Omega$ delivers a current through a load.

What is the maximum power delivered to the load?

- A** 5.0 W **B** 12.5 W **C** 25.0 W **D** 50.0 W