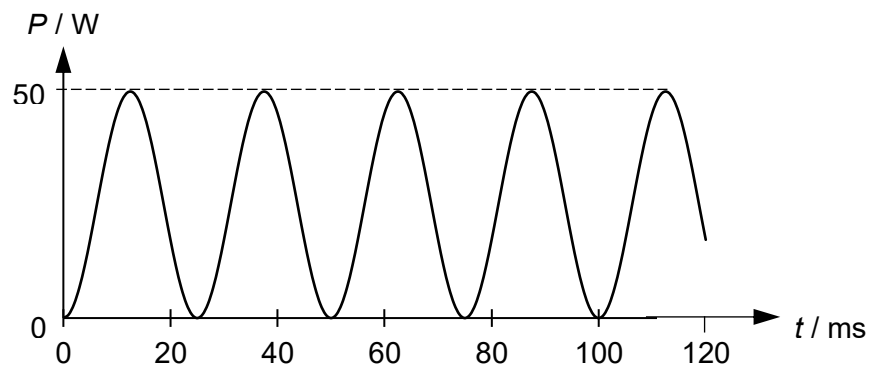


26 A sinusoidal alternating supply is connected to a  $10\ \Omega$  resistor in series. The graph shows how the power  $P$  dissipated across the resistor varies with time  $t$ .



What are the frequency  $f$  and the root-mean-square current  $I_{\text{r.m.s.}}$  of the alternating supply?

	$F / \text{Hz}$	$I_{\text{r.m.s.}} / \text{A}$
<b>A</b>	20	1.6
<b>B</b>	40	1.6
<b>C</b>	20	2.2
<b>D</b>	40	2.2