

- 26** A sinusoidal alternating current of peak value  $I_0$  passes through a resistor of resistance  $R$ . The mean power developed by the current in the resistor is  $P$ .

Another sinusoidal alternating current passes through a resistor of resistance  $2R$ . If the mean power developed by this current in it is  $4P$ , what is the root-mean-square value of this current?

- A**  $2.0 I_0$       **B**  $1.4 I_0$       **C**  $1.0 I_0$       **D**  $0.70 I_0$