

- 6 (a) Fig. 6.1 shows a potentiometer circuit for determining the resistance of resistor R. The uniform wire XY, of length 1.20 m, has a resistance of $20.0\ \Omega$. The balance length XJ is 0.48 m. At the balance length, a voltmeter connected across the $1.0\ \Omega$ resistor reads 0.50 V. Determine the resistance of resistor R.

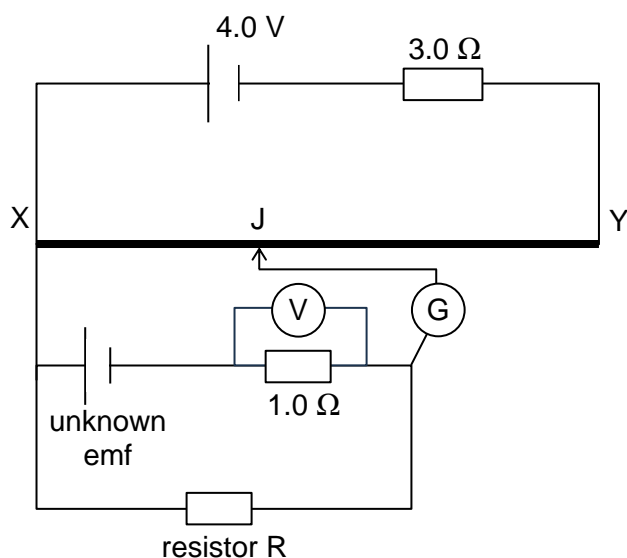


Fig. 6.1

resistance = Ω [3]

- (b) A copper wire has a length of 3.0 m and a uniform cross-sectional area of $0.20\ \text{mm}^2$. It carries a current of 2.8 A when a potential difference of 0.72 V is applied across it.
- (i) Given that the charge carrier in the copper wires are electrons, and that the number density of electrons is $8.49 \times 10^{28}\ \text{m}^{-3}$, determine its drift velocity.

velocity = m s^{-1} [2]

- (ii) Determine the resistivity of the copper wire.

resistivity = $\Omega \text{ m}$ [2]

- (iii) Explain, in microscopic terms, why the resistance of the copper wire increases as the current through it increases.

.....
.....
.....
..... [2]