

- 25** When an alternating current,  $I = I_0 \cos \omega t$ , passes through a resistor, the mean power dissipated in the resistor is  $P$ .

The peak value of the alternating current is then reduced by half and the current is passed through a diode.

What is the mean power dissipated in the resistor in terms of  $P$ ?

- A**  $\frac{P}{8}$                       **B**  $\frac{P}{4}$                       **C**  $\frac{P}{2}$                       **D**  $P$