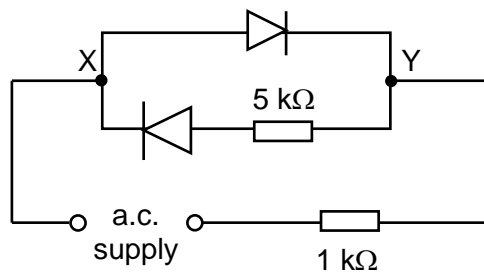


27 The figure below shows an a.c. supply connected to resistors and diodes.



Which of the following graphs represents the variation of current with time through XY of the circuit?

