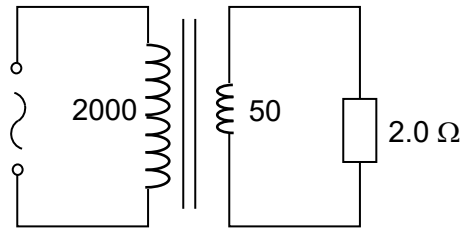


- 25** In the circuit shown, the **average** power dissipated across a $2.0\ \Omega$ resistor is $50\ \text{W}$. The turns ratio of the primary coil to secondary coil of the ideal transformer in the circuit is $2000 : 50$.



What is the peak potential difference across the primary coil of the ideal transformer?

- A** $20\ \text{V}$ **B** $40\ \text{V}$ **C** $400\ \text{V}$ **D** $564\ \text{V}$