

6

The circuit is used to supply energy to the battery from the generator. A variable resistor of resistance R is used to control the current in a circuit, as shown in Fig. 6.1.

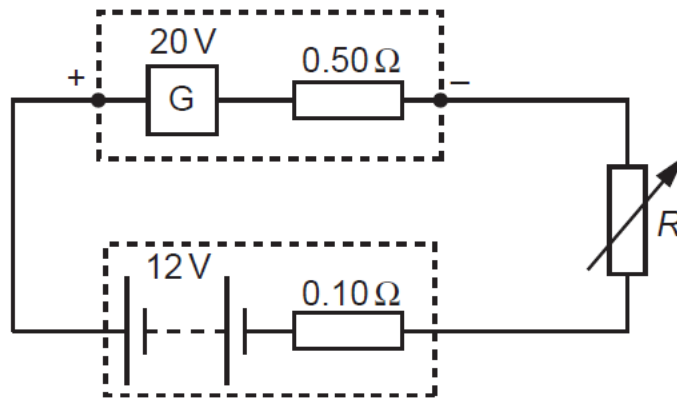


Fig. 6.1

The generator G has e.m.f. 20 V and internal resistance $0.50\ \Omega$. The battery has e.m.f. 12 V and internal resistance $0.10\ \Omega$. The current in the circuit is 2.0 A .

(a) Determine the resistance R .

resistance $R = \dots\dots\dots\ \Omega$ [2]

(b) Calculate the total power generated by G

power = $\dots\dots\dots\text{ W}$ [2]

(c) Calculate the power loss in the total resistance of the circuit.

Power loss = W [2]

(d) Determine the efficiency of the circuit.

efficiency = [3]

(e) A student suggests that the value of resistance R will not affect the efficiency calculated in **(d)**. Explain if you agree with the student.

.....

..... [1]

[Total: 10]

