
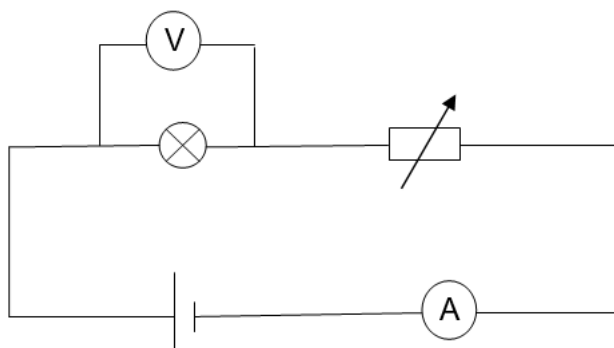


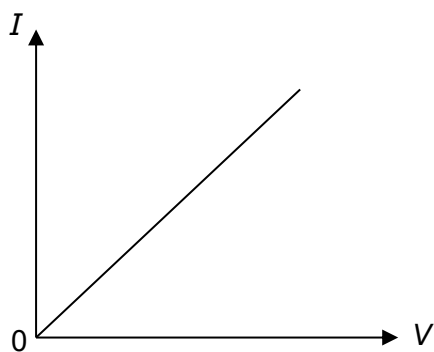22 In the circuit shown below, the current can be varied by means of the rheostat.




Which one of the following graphs best shows how the ammeter reading I varies with the voltmeter reading V ?


A



B

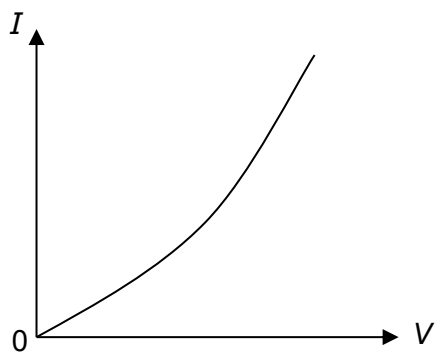

C

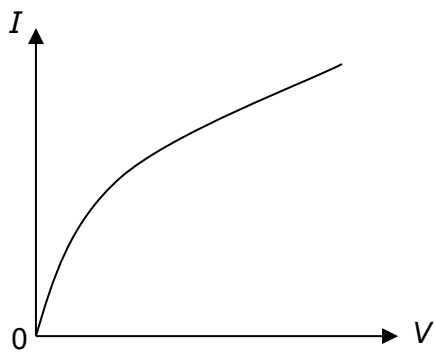

D

