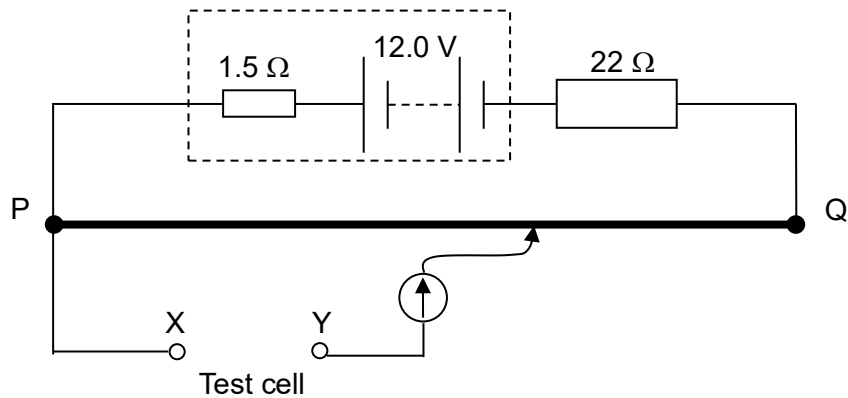


- 21 A student attempts to measure the e.m.f. of a test cell using a potentiometer circuit as shown in the diagram.



The wire PQ has a resistance of  $3.0\ \Omega$  and the driver cell has an e.m.f. of  $12.0\ \text{V}$ . He was unable to obtain an observable balance length on PQ when he connected the circuit. The tutor he consulted told him that the test cell has an e.m.f. of a few millivolts. What could he do in order to obtain an observable balance length?

- A Reversed the polarity of the test cell at XY.
- B Use a driver cell of e.m.f.  $20\ \text{V}$ .
- C Change the resistance of the connected resistor to  $1\ \text{k}\Omega$ .
- D Change the wire PQ to a wire of resistance  $20\ \Omega$ .