

- 5 (a) A thermistor and a filament bulb are connected in parallel to a battery as shown in Fig 5.1. The e.m.f.  $E$  of the battery is unknown and its internal resistance is negligible.

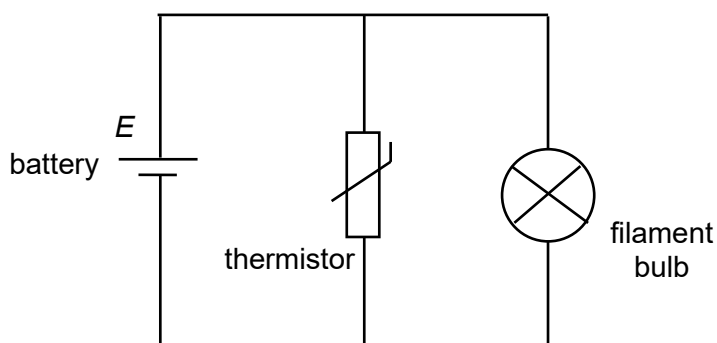


Fig 5.1

Fig. 5.2 shows the current-voltage ( $I$ - $V$ ) characteristics of the filament bulb and the thermistor.

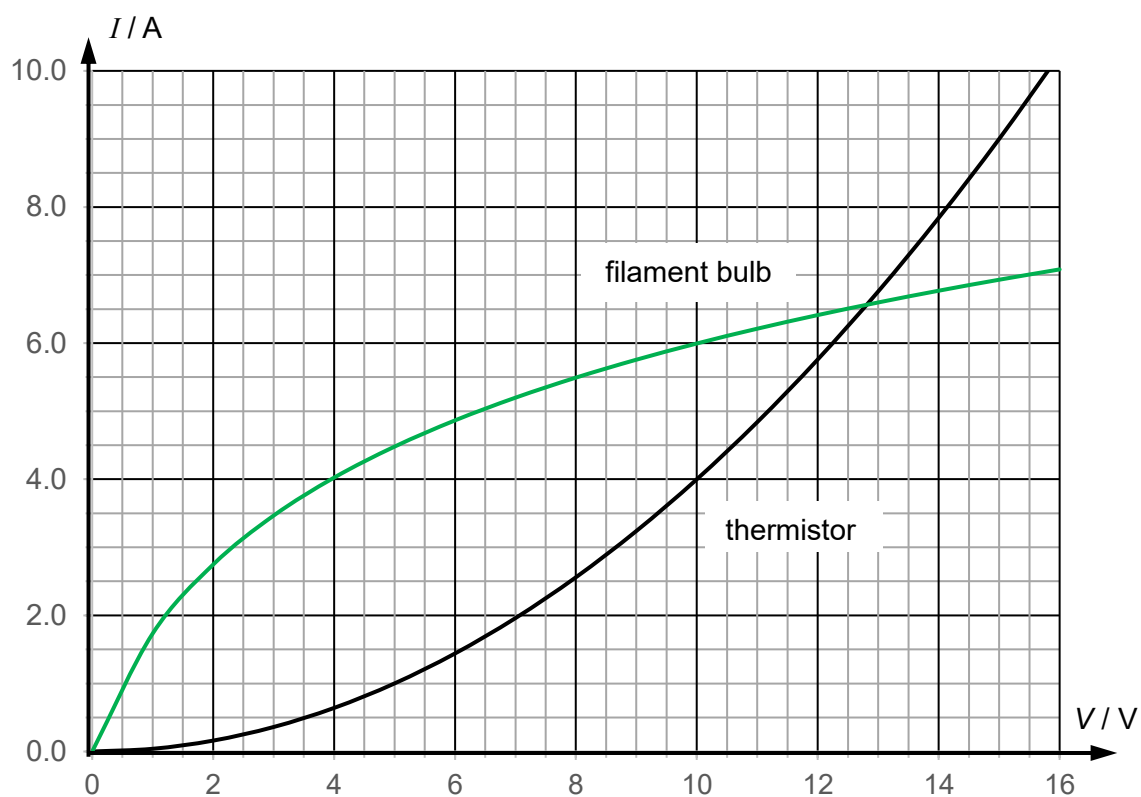


Fig 5.2

- (i) Describe the main features of Fig. 5.2 that show the characteristics of the negative temperature coefficient thermistor in terms of current, voltage and resistance.

.....  
 .....  
 .....  
 ..... [2]

- (ii) The current through the battery is 8.0 A.

Using Fig. 5.2, determine

1. the current through the filament bulb and the thermistor


current through the filament bulb = ..... A [1]

current through the thermistor = ..... A [1]

2. the e.m.f. of the battery.


e.m.f. = ..... V [1]

- (b) The filament bulb is now connected in series with a fixed resistor of  $2.5\ \Omega$  and a battery, as shown in Fig 5.3. The e.m.f.  $E$  of the battery is 14.0 V and its internal resistance is negligible.

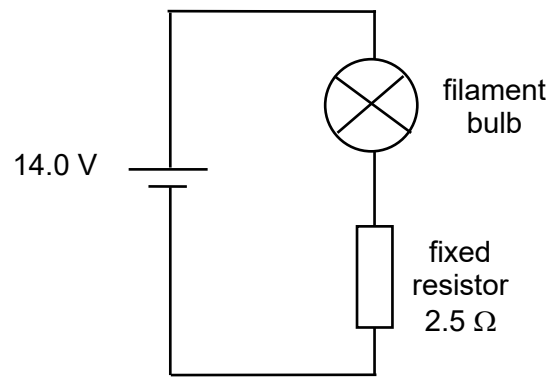

**Fig. 5.3**

The variation with the potential difference  $V$  of the current  $I$  for the filament bulb is shown in Fig. 5.4.

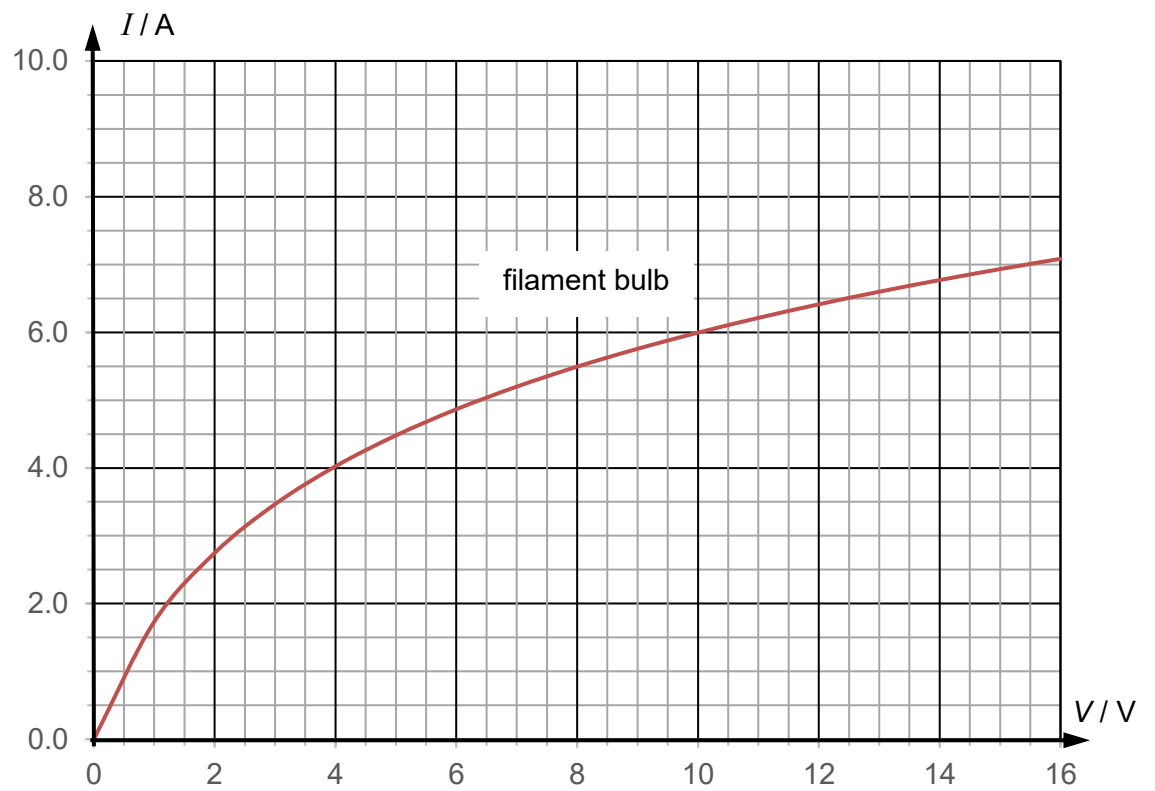

**Fig 5.4**

- (i) On Fig 5.4, draw a line to show the variation with the potential difference  $V$  of the current  $I$  through the fixed resistor. [1]
- (ii) Using Fig. 5.4, determine the current through the filament bulb.

current = ..... A [1]

- (iii) Using Fig. 5.4, determine the potential difference across the fixed resistor.

potential difference = ..... V [1]

[Total: 8]