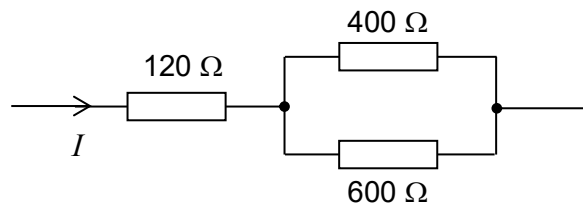


- 21** Three resistors are arranged in a part of a circuit, and the resistance of each resistor is labelled as shown.



The current through the  $120\ \Omega$  resistor is  $I$ .

What is the value of  $\frac{\text{power dissipated in the } 120\ \Omega \text{ resistor}}{\text{power dissipated in the } 600\ \Omega \text{ resistor}}$ ?

- A** 0.20                      **B** 0.50                      **C** 1.3                      **D** 5.0

