

		non-uniformly.
22	A	If the broken third bulb is the only fault, the voltmeter would show the reading of the e.m.f. of the supply.
23	B	Even if all three bulbs are in the same circuit, the voltmeter will read the e.m.f. of the supply.