

26 A generator produces 100 kW of power at a potential difference of 10 kV. The power is transmitted through cables of total resistance $5.0\ \Omega$.

How much power is dissipated in the cables?

A 50 W

B 250 W

C 500 W

D 50 000 W

27 A clean plate made of metal with work function energy of 2.36 eV is illuminated with