

5	(a)	$E = I(R + r)$ $9.0 = 0.450(18 + r)$ $r = 2.0 \, \Omega$	M1 A1
	(b)	$Q = It$ $= 0.450 \times 3600$ $= 1.6 \times 10^3 \, \text{C}$	M1 A1
	(c)	$E_{\text{total}} = IVt$ $= 0.450 \times 9.0 \times 3600$ $= 14.6 \times 10^3 \, \text{J}$	M1 A1
	(d)	$P = I^2 R$ $= (0.450)^2 \times 18.0$ $= 3.65 \, \text{W}$	M1 A1
	(e)	New effective resistance $= \frac{V}{I} = \frac{9.0}{0.225} = 40.0 \, \Omega$ Replacement resistance $= 40.0 - 2.0 = 38.0 \, \Omega$	M1 A1