

23	A	Option A is correct since resistance of A is $15\ \Omega$ while resistance of B is $10\ \Omega$. Option B is incorrect since power of A = $0.40\ \text{W}$ while power of B = $0.60\ \text{W}$. So power dissipated in B is only 1.5 times of that in A. Option C is incorrect since total current = $0.30 + 0.20 = 0.50\ \text{A}$ Option D is incorrect since at $0.20\ \text{A}$, A will have $2.0\ \text{V}$ across it while B will have $3.0\ \text{V}$ across it.
24	C	Assuming B is to the right