

	forward bias, the resistance is very low as seen by the near vertical line of the graph.
22	C No current flows through voltmeter. Hence $I_1 = I_2$. Current through ammeter = $I_1 = I_2$ Voltmeter reading = $R_1 I_2$ $= R_2 I_3$ $= E - I_4 R_3$
23	D