

26**C**

$$\frac{V_s}{V_p} = \frac{5}{1} \Rightarrow V_s = 5 \times 240 = 1200 \text{ V}$$

Current in the secondary circuit = $1200/1000 = 1.2 \text{ A}$

$$\frac{I_p}{I_s} = \frac{5}{1}$$

$$I_p = 5 \times 1.2 = 6.0 \text{ A}$$

6

27

B