

	Hence, by first law of thermodynamics, internal energy increases.	
5a	As current passes through the filament, <u>mobile charge carriers (electrons) transfer kinetic energy to the lattice ions</u> of the filament causing the filament to heat up gradually Filament produces light when it is at a <u>sufficiently high temperature</u> Heating process takes time and hence, full brightness is not immediately achieved.	B1 B1
5b	By potential divider principle, $V_{16\Omega} = \frac{16}{16+14} \times 12$ $= 6.4 \text{ V}$	C1 A1
5ci	$V_{\text{one lamp}} = 6.0 \text{ V}$ Potential difference across XY = $6.4 - 6.0$ = 0.4 V	A1

5cii	Point Y is at a higher potential.	A1
5d	Current through resistors = $\frac{12}{14+16}$ = 0.40 A Current through lamps = $0.50 - 0.40$ = 0.10 A	M1 A0
5e	$\frac{\text{total power dissipated by the lamps}}{\text{total power produced by battery}}$ $= \frac{VI_{\text{lamps}}}{VI_{\text{battery}}}$ $= \frac{12 \times 0.10}{12 \times 0.50}$ = 0.20	C1 A1
5f	No change to potential difference across lamps and hence (by $\frac{V^2}{R}$), power of lamps unchanged (Since effective resistance of circuit increases,) total current decreases and so power produced by battery decreases Ratio increases.	M1 A1
6a		