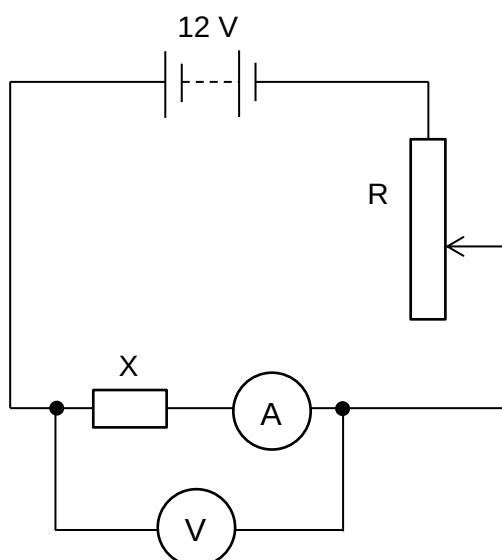


4	The variation with potential difference V of current I in a resistor X is shown in Fig. 4.1. Fig. 4.1		
	(a)	Use Fig. 4.1 to show that the resistance of X remains constant.	
			[2]
		<u>Method:</u> - calculate the <i>RATIO</i> of the <i>V</i>-coordinate to the <i>I</i>-coordinate. - Compare the ratios from the different points. Show that the ratios are constant. At (6.0 V, 1.25 A), $R = \frac{V}{I} = \frac{6.0}{1.25} = 4.8 \, \Omega$ At (12 V, 2.5 A), $R = \frac{V}{I} = \frac{12}{2.5} = 4.8 \, \Omega$ Since the ratio $\frac{V}{I}$ remains constant at 4.8 Ω, resistance of X remains constant. <u>Method 2:</u> - Calculate gradient with either 2 points that are far apart on the graph OR at least 3 different points along the graph. - Use the gradient and straight line equation to calculate y-intercept and show that it is equal to zero.	1 1 1 1
	(b)	In an attempt to obtain the graph of Fig. 4.1 for resistor X, a student sets up a circuit as shown in Fig. 4.2.	

**Fig. 4.2**

The battery has an e.m.f. of 12 V and negligible internal resistance. The resistor R has a resistance that can be varied between 0.0 Ω and 2.0 Ω . The voltmeter and ammeter are both ideal.

State and explain why the circuit shown in Fig. 4.2 is inappropriate for obtaining data from $V = 6 \text{ V}$ to $V = 12 \text{ V}$ for the graph in Fig. 4.1.

When R is set to its minimum of 0 Ω , a maximum potential difference (p.d.) of 12 V can be applied across X. Hence voltmeter and ammeter readings up to $V = 12 \text{ V}$ are obtainable.

However, when R is set to its maximum of 2.0 Ω , since X has resistance of 4.8 Ω which is greater than 2.0 Ω , the p.d. across X will be greater than 6 V ($\frac{4.8}{4.8+2.0} \times 12 = 8.5 \text{ V}$). It would thus be impossible to obtain voltmeter and ammeter readings in the range of $V = 6 \text{ V}$ to $V = 8.5 \text{ V}$ in Fig. 4.1.

[2]

1

1

(c) In the space below, draw a circuit diagram using the same components as shown in Fig. 4.2 from which the graph of Fig. 4.1 may be determined.

[1]

Solution:

			1
(d)	Calculate the difference in the power dissipated in resistor X when V is increased from 7.2 V to 9.6 V.		
		difference in power = W	[2]
	Solution: $\text{Difference in power} = I_1 V_1 - I_2 V_2$ $= (2.0)(9.6) - (1.5)(7.2)$ $= 8.4 \text{ W}$		1 1
(e)	Suppose the battery has an internal resistance of 0.50Ω , and R in Fig. 4.2 is adjusted to 0Ω . Calculate the terminal potential difference across the battery.		
		terminal potential difference = V	[2]
	By potential divider principle, $\text{terminal p.d.} = \text{p.d. across X} = \frac{4.8}{4.8 + 0.5} \times 12 \text{ V}$ $= 10.868 \text{ V} = \mathbf{11 \text{ V}}$		1 1

5 **(a)** When white light is incident on a single slit, a diffraction pattern is formed on a screen