
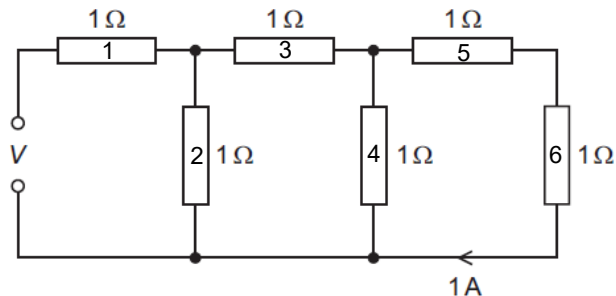


20

D

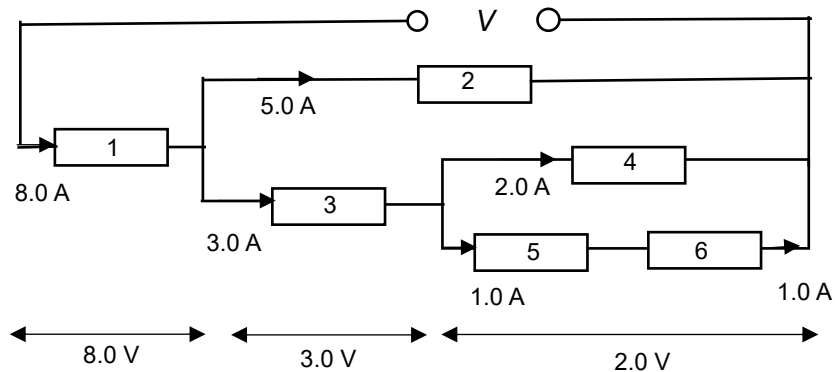

The above circuit when re-drawn is same as the circuit below



Then the currents and p.d. across the other resistors can be found.

$$V = 8.0 + 3.0 + 2.0 = 13.0 \text{ V}$$

21

A

The I-V graph for a filament lamp is as follows: