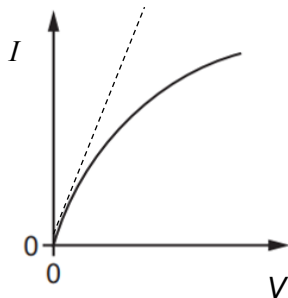


- 21** **A** The I-V graph for a filament lamp is as follows:



The corresponding V-I graph is a reflection of the graph about the dotted line.

- 22** **B** Resistors are connected in parallel, thus they have same p.d.