

25 **C** Current is able to flow both ways due to two diodes in opposite directions. One of the diodes is connected in series to another resistor, which reduces current in that direction.

26 **C** Since magnitude of emf is proportional to rate of change of flux when flux is