

as to produce an effect to oppose the increasing magnetic flux linkage)

27 B When current is forward bias for the single diode, the total resistance is $1\text{ k}\Omega$. The peak current = peak voltage / $1\text{ k}\Omega$.

When current is forward bias for the single diode in series with the $5\text{ k}\Omega$ resistor, the total resistance is $6\text{ k}\Omega$. The peak current = peak voltage / $6\text{ k}\Omega$. This is smaller than the previous case and the direction is opposite.

28 D
$$\lambda = \frac{hc}{E} = \frac{(6.63 \times 10^{-34})(3 \times 10^8)}{2.045 \times 10^{-15}} = 9.7 \times 10^{-10}\text{ m}$$