

Qn 4	Answer	Marks
(a)(i)	Power supplied by battery = Energy / time = (11.3 J) / (10 x 60 s) = 0.0188 W	M1 A1
(a)(ii)	From graph, resistance of thermistor = 3.1 kΩ Power dissipated through the resistor and thermistor = Power supplied by battery $\Rightarrow 0.0188 = E^2 / (3100 + 1200)$ $E = 8.99 \text{ V}$	B1 M1 A1
(b)	From graph, New resistance of thermistor = 2.0 kΩ Since the power delivered is the same, Total resistance before = total resistance after $\Rightarrow 3100 + 1200 = R + 2000$ $\Rightarrow R = 2300 \text{ } \Omega$	B1 M1 A1
	[Total : 8 marks]	