

22 (D)

For closed circuits, terminal p.d. is lower when there is internal resistance in the source (non-ideal).

23 (C)