

23 (C)

At X, voltmeter measure emf of battery.

At Y, voltmeter measure emf of battery. Voltmeter and lamp is connected in series.

At Z, it is a open circuit. Voltmeter reads 0 V.

24 (A)