

- 4 (a) (i) effective resistance across BN = $\left(\frac{1}{2R} + \frac{1}{R+R}\right)^{-1} = R$ M1
effective resistance across AM = $\left(\frac{1}{2R} + \frac{1}{R+R_{BN}}\right)^{-1} = \left(\frac{1}{2R} + \frac{1}{R+R}\right)^{-1}$ A0
= R
- or effective resistance across AM = $\left(\frac{1}{2R} + \frac{1}{R+\left(\frac{1}{2R} + \frac{1}{R+R}\right)^{-1}}\right)^{-1}$ (M1)
- (ii) use potential divider principle, $V_{AM} = \frac{R}{R+R} \times V = \frac{1}{2}V$ M1
- $V_A - V_M = V_A - 0 = V_{AM}$, so $V_A = \frac{1}{2}V$ A1
- (iii) $V_D = \frac{1}{2}V_C = \frac{1}{2} \times \frac{1}{2}V_B = \frac{1}{4} \times \frac{1}{2}V_A = \frac{1}{8} \times \frac{1}{2}V$ C1
- $V_D = \frac{1}{16}V$ A1
- (b) either $R_P = \frac{6}{6 \times 10^{-3}} (= 1000 \Omega)$ C1
- $R_Q = \frac{6}{3 \times 10^{-3}} (= 2000 \Omega)$ C1
- $R_{MN} = \left(\frac{1}{1000} + \frac{1}{2000}\right)^{-1} = 667 \Omega$ A1
- or p.d. across MN = 6 V (C1)
- total current = 6 + 3 = 9 mA (C1)
- $R = \frac{6}{9 \times 10^{-3}} = 667 \Omega$ (A1)

5 (a) (i) region of space which a force is felt/experienced

B1